American Computer Science League

2020-2021 • Contest 4: Shorts • Junior Division


1. Graph Theory

Given the set of vertices: {A, B, C, D, E} and the set of directed edges: {AB, BE, AD, EA, CB, DB, BA, BC}, how many paths are there of length 2 from Vertex B?

- A. 1
- B. 2
- C. 3
- D. 4
- E. 5

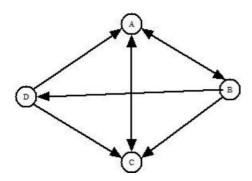2. Graph Theory


Given the following directed graph, how many cycles are there from A?



- A. 7
- B. 6
- C. 5
- D. 4
- E. 3

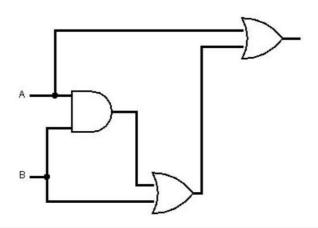3. Digital Electronics


Simplify the Boolean expression represented by the following digital circuit:



- A. A
- B. A+B
- C. B
- D. AB
- E. 1

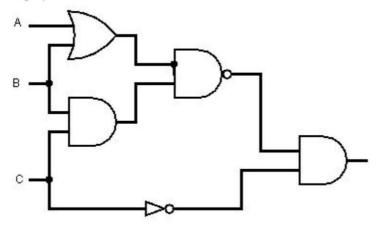4. Digital Electronics

Identify all possible ordered triples that make the following digital circuit TRUE.



- A. (*,*,0)
- B. (*,0,1)
- C. (*,*,1)
- D. (0,*,1)
- E. (0,*,*)

5. What Does This Program Do? (Strings)

What is the length of the longest substring of B in which the elements are in ascending alphabetical order?

- a = "FOURTHACSLCONTEST"
- b = ""

for x = 1 to len(a) - 2

if a[x] > "O" then

b = b + a[x+1]

end if

if a[x] < "0" then

b = a[x-1] + b

end if

next x

A. 2

B. 3

C. 4

D. 5

E. 6

American Computer Science League

2020-2021 • Contest 4: Shorts • Junior Division


1. Graph Theory

给定项点集合: {A, B, C, D, E} 和有向边集合: {AB, BE, AD, EA, CB, DB, BA, BC}, 请问从项点 B 出发有多少条长度为 2 的路径?

- A. 1
- B. 2
- C. 3
- D. 4
- E. 5

2. Graph Theory


给定以下有向图,请问从A出发有多少个环?

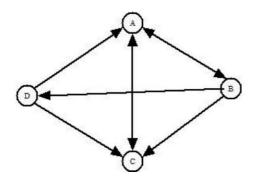

- A. 7
- B. 6
- C. 5
- D. 4
- E. 3

3. Digital Electronics


化简下述用数字电路表示的布尔表达式:

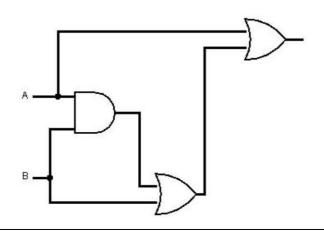

- A. A
- B. A+B
- C. B
- D. AB
- E. 1

4. Digital Electronics

请找出所有可以使下述数字电路为真的有序三元组。

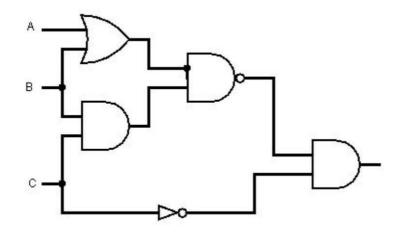

A. (*,*,0)

B. (*,0,1)

C. (*,*,1)

D. (0,*,1)

E. (0,*,*)

5. What Does This Program Do? (Strings)

元素按字母升序排列时, B 的最长子串长度是多少?

a = "FOURTHACSLCONTEST"
b = ""
for x = 1 to len(a) - 2
 if a[x] > "0" then
 b = b + a[x+1]
 end if
 if a[x] < "0" then
 b = a[x-1] + b
 end if
next x</pre>

A. 2

B. 3

C. 4

D. 5

E. 6