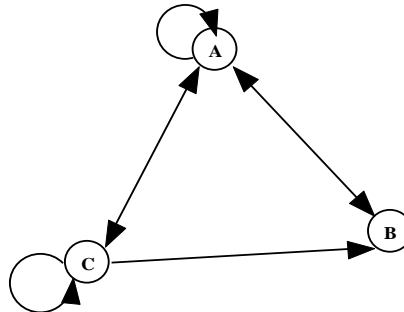


考号/Exam Code: _____ 姓名/Name: _____ 学校/School: _____

1. Graph Theory


How many paths of length 3 are there in the directed graph at the right?



1.

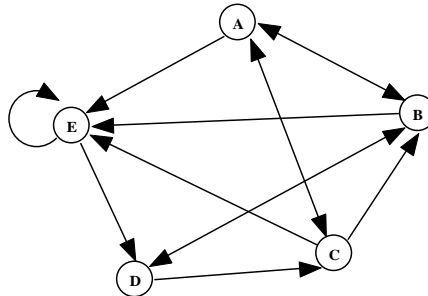2. Graph Theory


How many cycles are there from A in the directed graph at the right?



2.

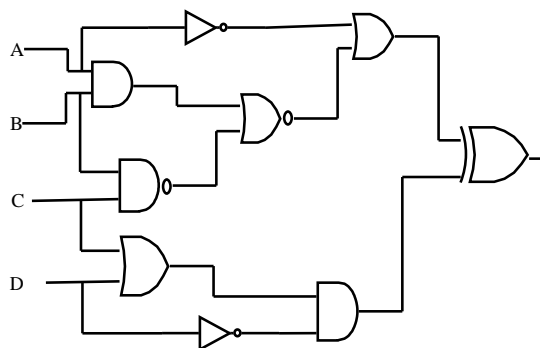3. Digital Electronics


Translate the digital circuit into the Boolean expression it represents. Do not simplify.



3.

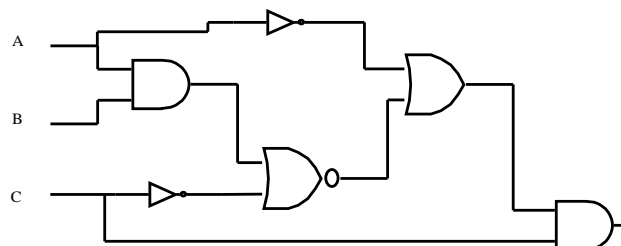4. Digital Electronics

How many ordered triples make the digital circuit TRUE?



4.

INTERMEDIATE DIVISION**5. Assembly Language**

What is output after this program is executed?


```
A   DC   36
LOAD  A
DIV   = 10
STORE B
MULT  = 10
STORE C
LOAD  A
SUB   C
STORE D
MULT  = 10
ADD   B
STORE E
SUB   A
DIV   = 9
STORE G
PRINT G
END
```

5.

考号/Exam Code: 姓名/Name: 学校/School:

1. Graph Theory


在右边的有向图中，有多少条长度为 3 的路径？

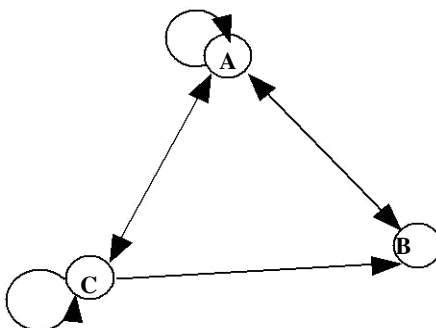

1.

2. Graph Theory


在右边的有向图中，从 A 开始的循环有多少个？

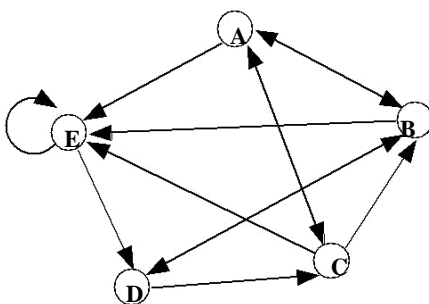

2.

3. Digital Electronics


将数字电路转换成其等效布尔表达式。不要简化。

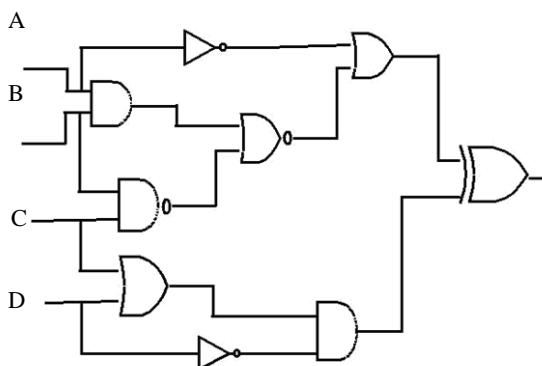

3.

4. Digital Electronics

有多少有序三元组使
右边的数字电路为真?

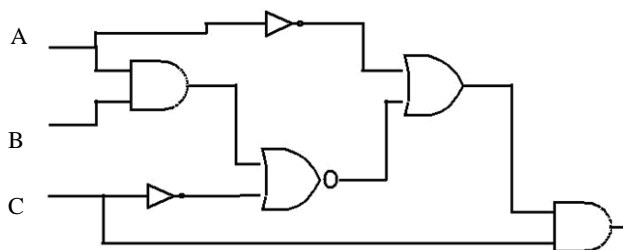

4.

American Computer Science League

2018-2019

Contest #4

INTERMEDIATE DIVISION

5. Assembly Language

执行此程序后，输出是什么？

```
A DC    36
LOAD    A
DIV     = 10
STORE   B
MULT    = 10
STORE   C
LOAD    A
SUB     C
STORE   D
MULT    = 10
ADD     B
STORE   E
SUB     A
DIV     = 9
STORE   G
PRINT   G
END
```

5.