

JUNIOR DIVISION


考号/Exam Code: _____

姓名/Name: _____


学校/School: _____

1. Graph Theory


Draw the adjacency matrix for the directed graph at the right?

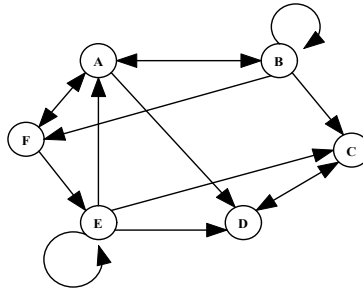**1.****2. Graph Theory**


How many paths of length 2 are there in the directed graph at the right?

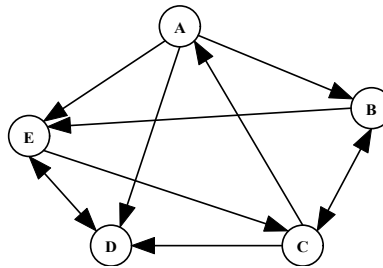**2.****3. Digital Electronics**

Which ordered pairs make the digital circuit at the right TRUE?

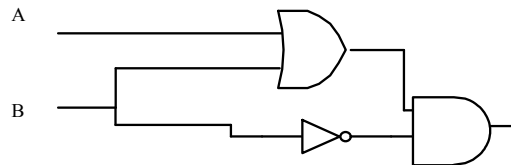**3.****4. Digital Electronics**

Translate the digital circuit at the right to its equivalent Boolean expression.

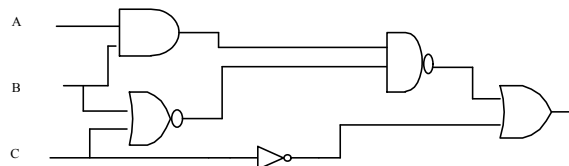**4.**

JUNIOR DIVISION

5. What Does This Program Do? - Strings

What is the output when this program is run?

```
A="NEWJERSEYISTHEGARDENSTATE"
B="": C="": D="": E="": F=""
for x = 0 to len(A) - 1
    if A[x, x] < "K" then
        B = B + A[x, x]
    else
        C = C + A[x, x]
    end if
next x
for x = 0 to len(B) - 1
    if B[x, x] != "E" then
        D = D + B[x, x]
    end if
    if C[x, x] != "S" then
        E = E + C[x, x]
    end if
next x
for x = 0 to 5
    if ((D[x, x] != "A") && (E[x, x] != "R")) then
        F = D[x, x] + F + E[x, x]
    end if
next x
output F
end
```

5.


考号/Exam Code: _____

姓名/Name: _____


学校/School: _____

1. Graph Theory


画出右边有向图的邻接矩阵。

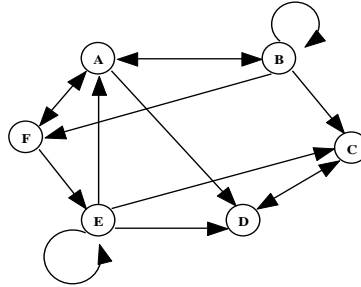**1.****2. Graph Theory**


在右边的有向图中，有多少条长度为 2 的路径？

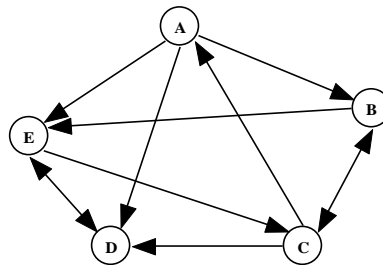**2.****3. Digital Electronics**

哪些有序对使右边的数字电路为真？

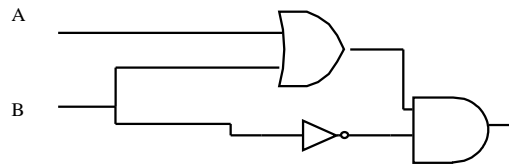**3.****4. Digital Electronics**

将右边的数字电路转换为其等效的布尔表达式。

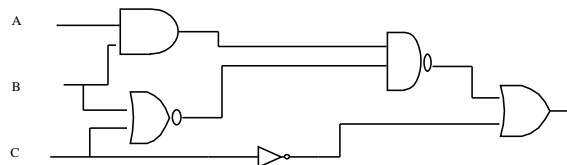**4.**

JUNIOR DIVISION

5. What Does This Program Do? - Strings

执行此程序后，输出是什么？

```
A="NEWJERSEYISTHEGARDENSTATE"
B=""; C=""; D=""; E=""; F=""
for x = 0 to len(A) - 1
    if A[x, x] < "K" then
        B = B + A[x, x]
    else
        C = C + A[x, x]
    end if
next x
for x = 0 to len(B) - 1
    if B[x, x] != "E" then
        D = D + B[x, x]
    end if
    if C[x, x] != "S" then
        E = E + C[x, x]
    end if
next x
for x = 0 to 5
    if ((D[x, x] != "A") && (E[x, x] != "R")) then
        F = D[x, x] + F + E[x, x]
    end if
next x
output F
end
```

5.